

# PROJECT 01

ECE 317

Kai Brooks

Lab TA: N/A



Electrical and Computer Engineering  
Portland State University  
2019-10-15

Contents

<b>1</b>	<b>Circuit 1</b>	<b>1</b>
1.1	Circuit Diagram . . . . .	1
1.2	Output . . . . .	2
<b>2</b>	<b>Circuit 2</b>	<b>4</b>
2.1	Circuit Diagram . . . . .	4
2.2	Output . . . . .	4
<b>3</b>	<b>Circuit 2</b>	<b>5</b>
3.1	Circuit Diagram . . . . .	5
3.2	Output . . . . .	6

# 1    Circuit 1

## 1.1    Circuit Diagram

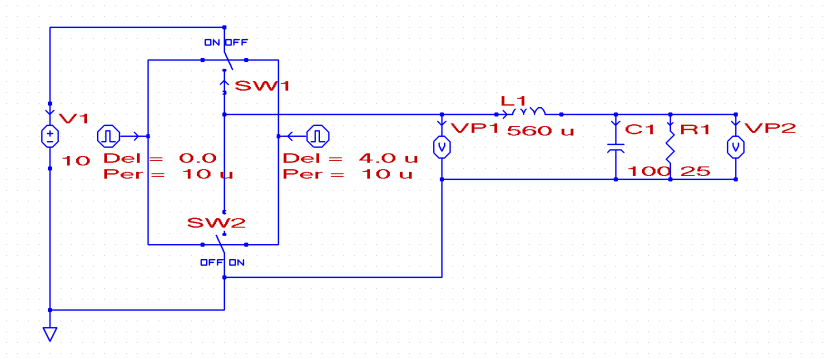


Figure 1: Circuit

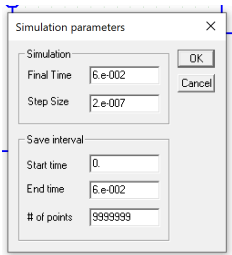


Figure 2: Simulation Parameters

1.2 Output

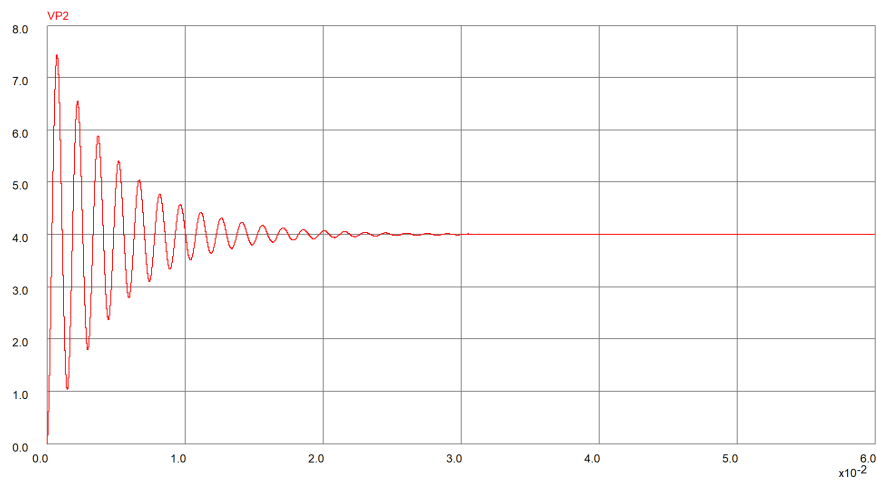


Figure 3: Full waveform

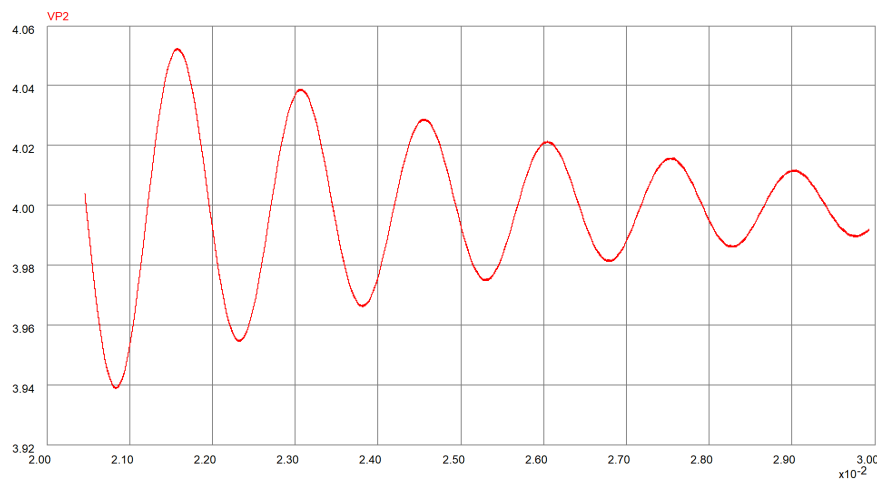


Figure 4: Zoomed waveform

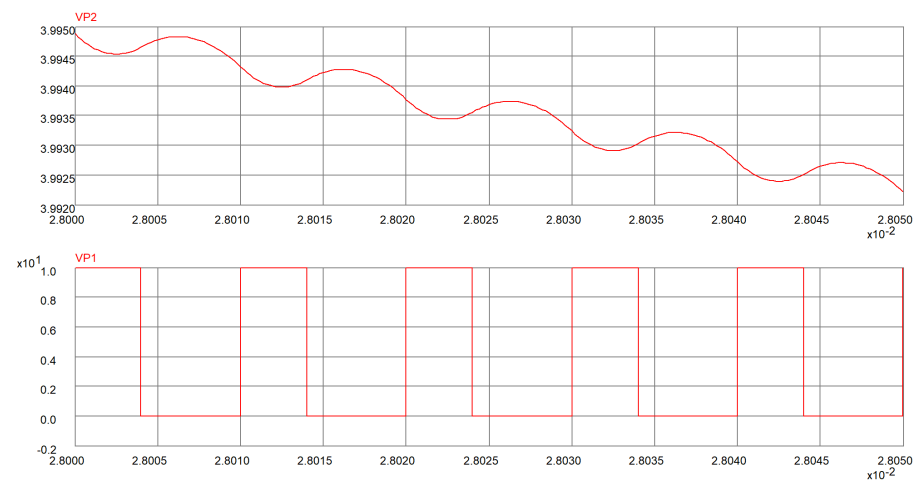


Figure 5: Comparative waveform

Peak Amplitude	Period	Pulse Width	Duty Ratio
10v	10 $\mu$ s	4 $\mu$ s	0.4

Table 1: Circuit 1 calculations

## Question

Taking the above plots into consideration, explain why you would expect to get the steady state value you found above?

## Answer

$$\text{Steady State} = \text{Peak Amplitude} \cdot \text{Duty Ratio} \quad (1)$$

It is expected to get the steady state above as the peak voltage is 10v and the duty ratio is 0.4.

## 2 Circuit 2

### 2.1 Circuit Diagram

Figure 6: Circuit

Figure 7: Simulation Parameters

### 2.2 Output

Figure 8: Comparative waveform

Peak Amplitude	Period	Pulse Width	Duty Ratio
$10v$	$10\mu s$	$4\mu s$	0.4

Table 2: Circuit 2 calculations

### Question

*Given that  $K_1 = -1$ , what other factors in the circuit determines the peak amplitude and why?*

### Answer

$$\text{Steady State} = \text{Peak Amplitude} \cdot \text{Duty Ratio} \quad (2)$$

It is expected to get the steady state above as the peak voltage is  $10v$  and the duty ratio is 0.4.

## 3 Circuit 2

### 3.1 Circuit Diagram

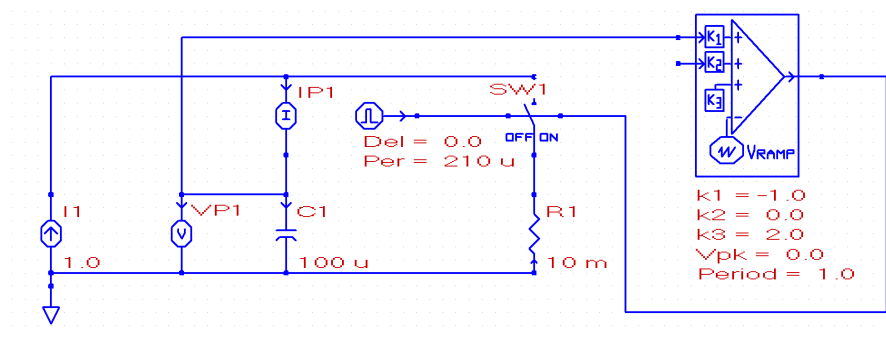


Figure 9: Circuit

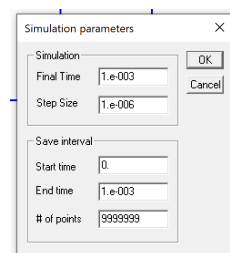


Figure 10: Simulation Parameters

## 3.2 Output

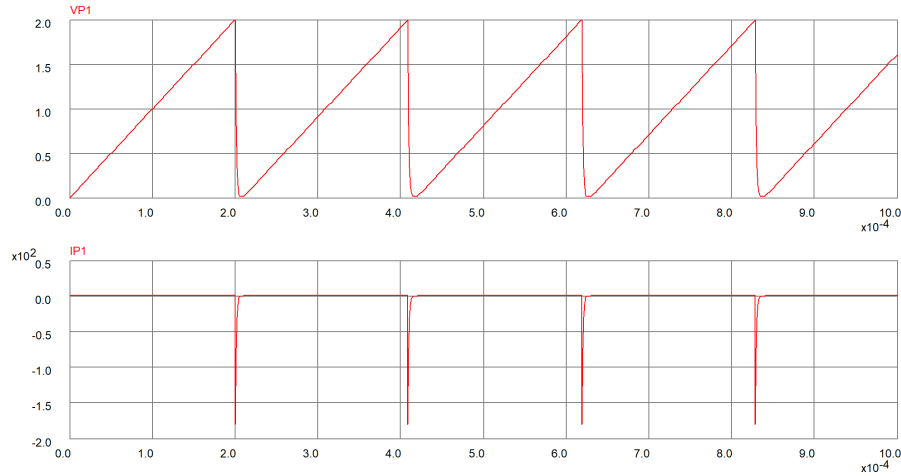


Figure 11: Comparative waveform

	Switching Fre- quency	Duty Ratio	Peak-to- peak Input Voltage to Filter	Steady State Average Output Voltage	Peak-to- peak Output Voltage Ripple
<b>Circuit 1</b>					
<b>Circuit 3</b>					

Table 3: Comparative omnibus

## Question

*Explain the differences seen in the peak-to-peak ripple voltage values between Circuit 3 and Circuit 1. Are they in line with your expectations? Why?*

## Answer

The ripple is smaller in circuit 3 because the capacitor is being charged and discharged more frequently. This results in a smaller ripple voltage as seen in the above plots.